



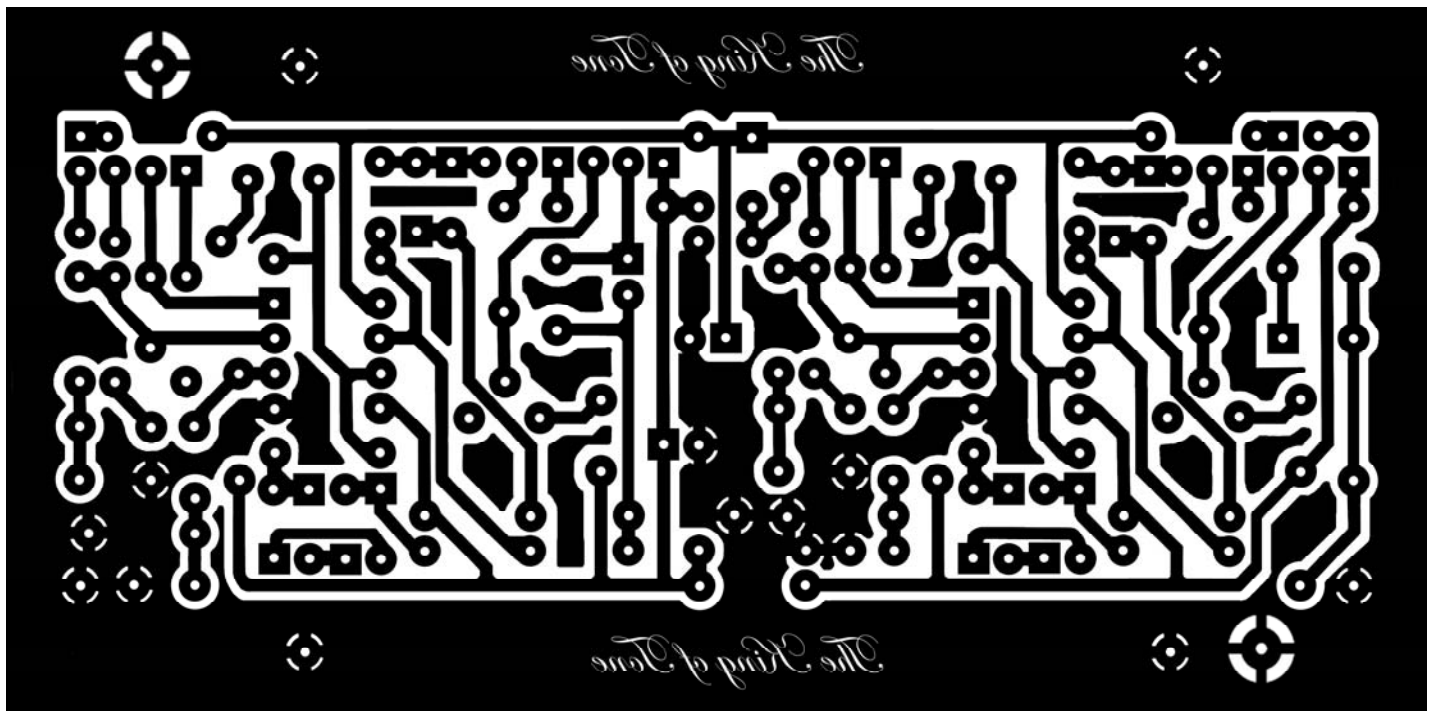


# King of Tone

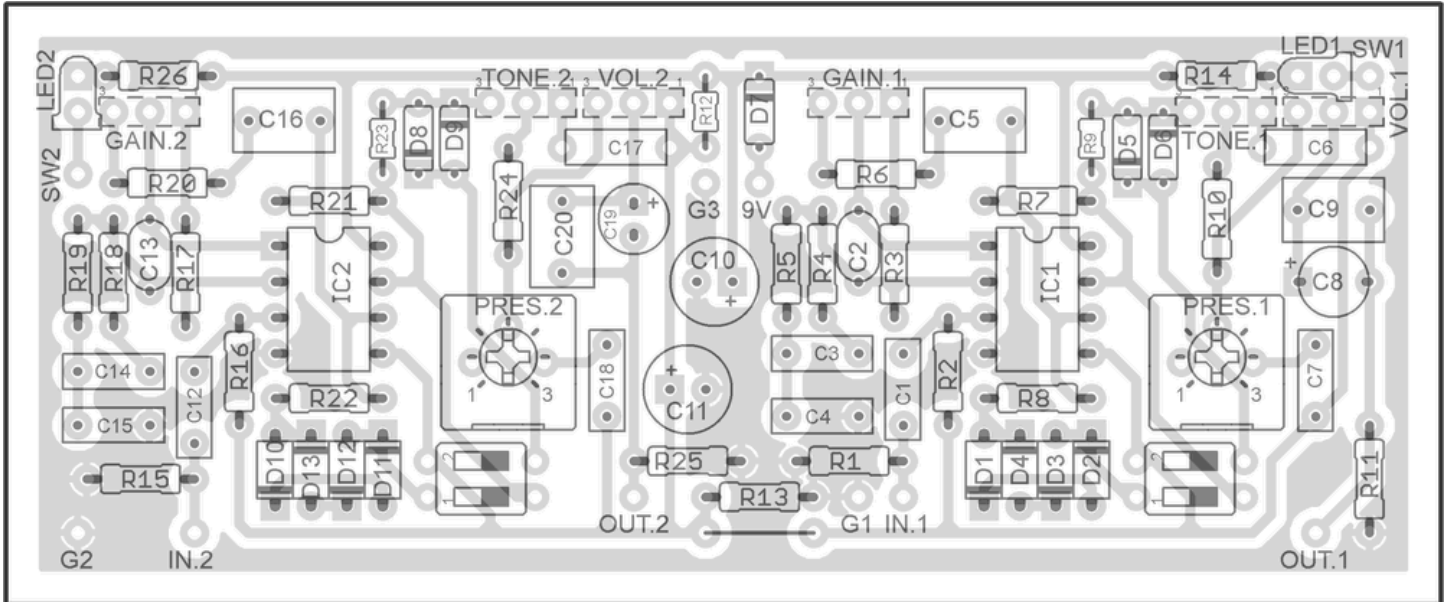

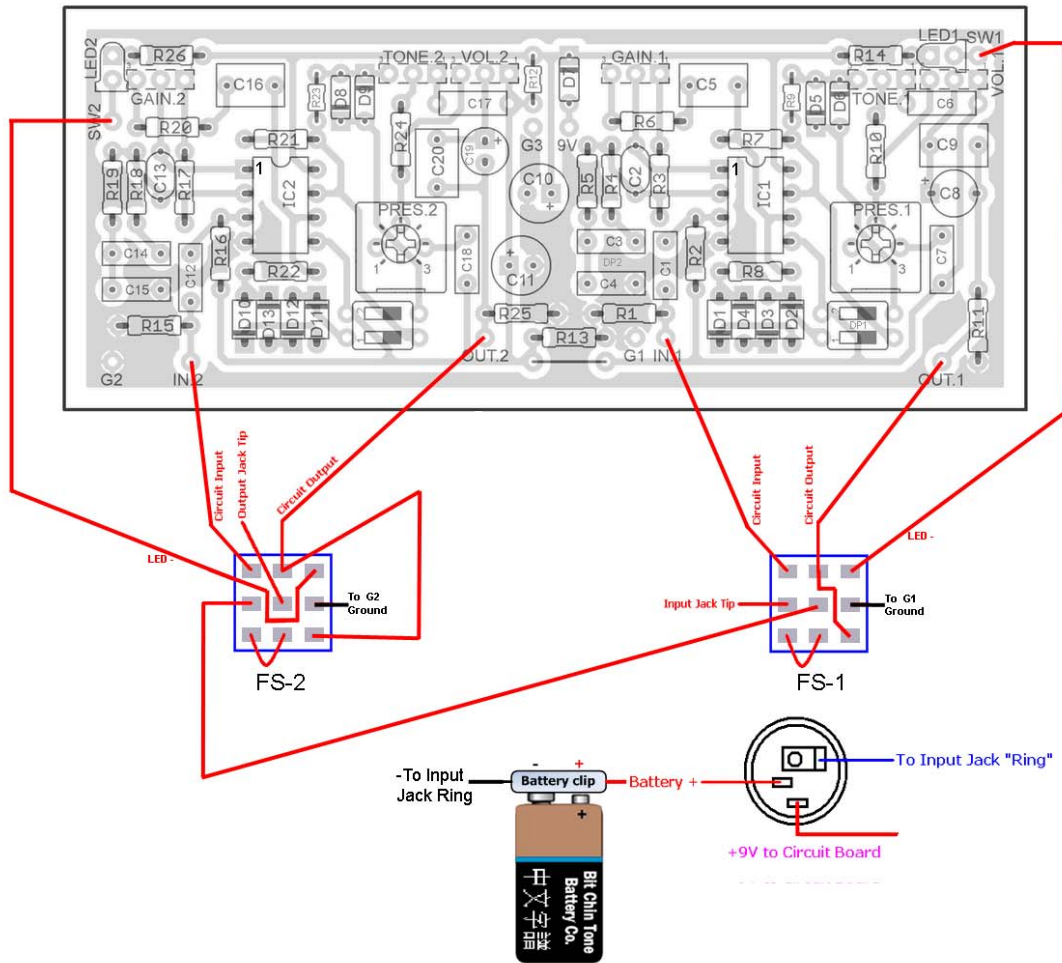

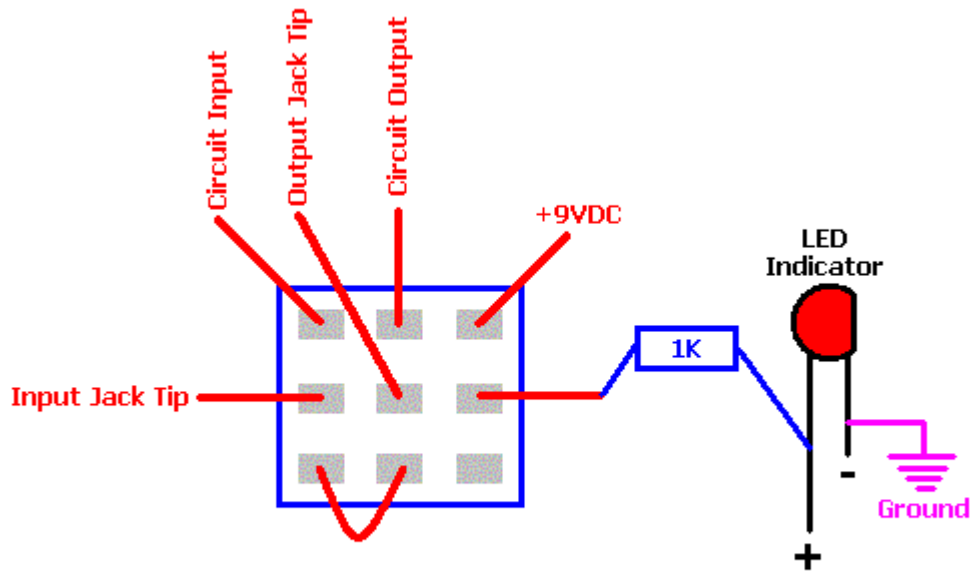

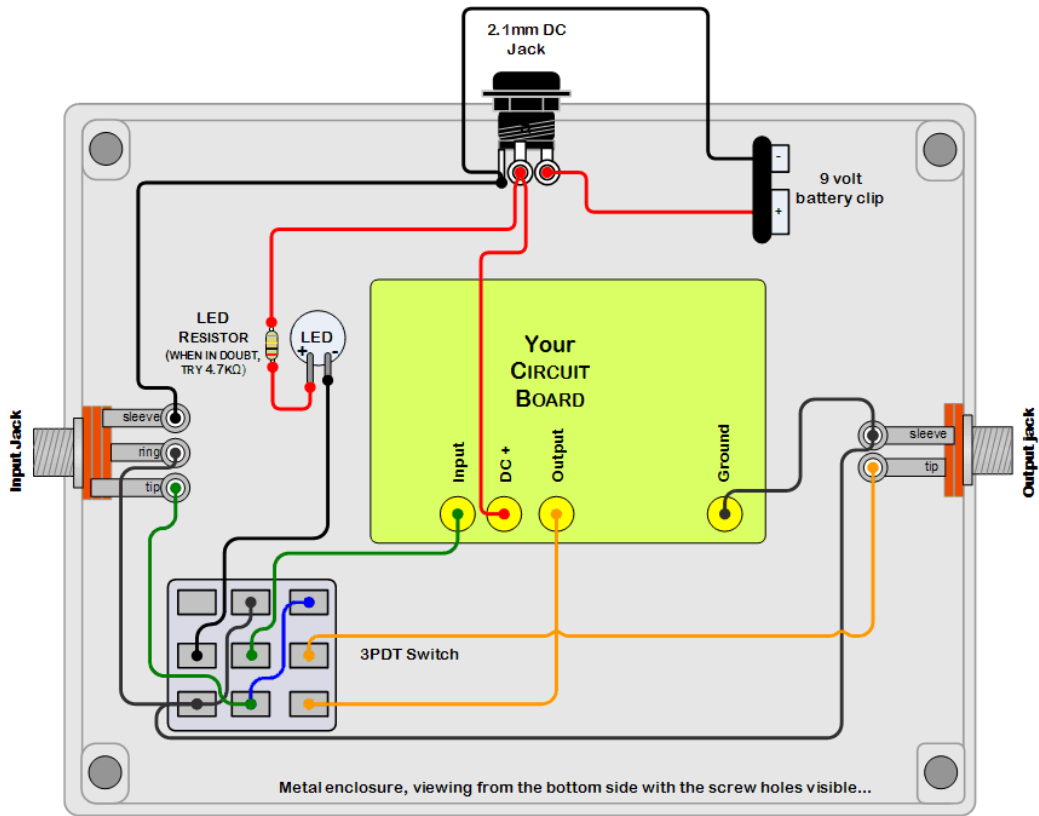

**3PDT switch wiring for a NPN pedal**